

Selen Görgün

21802674

CS 223-3

Lab 4 Preliminary Report

Circuit schematic for the internal design of the multifunctional register :

